

CONTENTS

	PAGE
PREFACE TO THE SECOND EDITION	vii
ACKNOWLEDGMENTS	viii
PREFACE TO THE FIRST EDITION	ix
CHAPTER 1	
PHYSICAL CONCEPTS	1
Excitation, Ionization, and Radiation	1
Excitation and Ionization Potentials	3
Types of Ionization	4
Ionization by Collision	4
Photoionization	5
Space Charge and Space Current	6
Deionization	6
Emission of Electrons and Other Ions from Solids	9
Electron Dynamics	11
Motion of Electrons in Electric Fields	11
Motion of Electrons in Magnetic Fields	15
Problems	17
CHAPTER 2	
THERMIONIC EMISSION: THE HIGH-VACUUM THERMIONIC DIODE	19
Theory of Thermionic Emission	19
Richardson's Equation	21
Tungsten and Thoriated Tungsten Emitters	23
Oxide-coated Emitters	26
Cesiated Tungsten Emitters	28
Mechanical Structure of Cathodes	29
Effects of Gas upon Emission and Space Currents	30
Limitation of Anode Current by Space Charge	32
Child's Law	33
Deviations from Child's Law Observed in Practical Diodes	35
Classification of Tubes	37
Structure of Typical Glass and Metal Tubes	41
Bibliography	42
CHAPTER 3	
GRID-CONTROLLED HIGH-VACUUM TUBES	43
Theory of Grid Action in Triodes	44
Functional Equations for Plate and Grid Currents	45
Time of Transit of Electrons	47
Static and Dynamic Characteristics	47
Tube Factors	50

	PAGE
Relation of Tube Factors to Characteristic Curves	54
Sharp-cutoff and Remote-cutoff Grids. Variable- μ Tubes	55
The Screen-grid Tetrode	56
The Space-charge Tetrode	58
The Suppressor Pentode	59
The Beam Pentode	63
Applied Voltages in Grid and Plate Circuits	66
Form of Alternating Plate-current Wave	66
Symbols for Electrode Voltages and Currents	68
Current and Voltage Relations in the Grid and Plate Circuits	71
Static and Dynamic Operating Points	72
Series Expansion for Alternating Plate Current	74
Harmonic Generation and Intermodulation	77
Relation of Series Coefficients to Dynamic Tube Characteristics	81
Dynamic Plate Resistance	84
Problems	85

CHAPTER 4

METHODS OF ANALYSIS OF VACUUM TUBES AND VACUUM-TUBE CIRCUITS	87
The Equivalent Plate Circuit	87
Construction of Equivalent Plate Circuits	89
Equivalent Circuits for Electrodes Other than the Plate	92
Tube Capacitances and Admittances	93
Static Load Line	97
Dynamic Path of Operation. Dynamic Load Line	99
The Plate Diagram	100
Plate Diagram for a Load Having Equal A-c and D-c Resistances	102
Simplified Plate Diagram for a Load Having Unequal A-c and D-c Resistances	102
Exact Plate Diagram for Loads Having Unequal A-c and D-c Resistances	103
Graphical Analysis of Plate Current	106
Formulas for Graphical Analysis	107
Percentage Harmonic and Distortion Factor	115
Construction of the Plate Diagram	115
Graphical Determination of Power Output	117
Dynamic Grid Characteristics	118
Starting and Stopping Transients	119
Problems	121
Supplementary Bibliography	123

CHAPTER 5

AMPLIFIER DEFINITIONS, CLASSIFICATIONS AND CIRCUITS	124
Amplifier Distortion	124
Amplifier Classification	127
Amplifier Circuits	128
Use of Cathode Resistors to Provide Bias	131
Push-pull Amplifiers	133
Frequency Range of Amplifiers	138
Class A, Class AB, Class B, and Class C Amplifiers	139
The Decibel	141

CHAPTER 6

	PAGE
ANALYSIS AND DESIGN OF VOLTAGE AND CURRENT AMPLIFIERS	144
Voltage Amplification of Tube with Impedance Load	144
Voltage Amplification of Direct-coupled Amplifiers	147
Impedance-capacitance-coupled Voltage Amplifier	147
Resistance-capacitance-coupled Amplifier	149
Effect of Circuit Constants upon Resistance-capacitance-coupled Amplifier Response	155
Practical Considerations in the Design of Resistance-capacitance-coupled Audio Amplifiers	156
Design Procedure for Resistance-capacitance-coupled Voltage Amplifiers	158
Effect of Plate Supply Filter and of Self-biasing Impedance	161
Compensated Amplifiers	162
The Cathode-follower Amplifiers	164
Filter-type Wide-band Amplifiers	174
Transformer-coupled Audio Amplifier	174
Control of Amplification of Audio-frequency Amplifiers	185
Volume Compression and Expansion	186
Tone Control	187
Tuned Radio-frequency Amplifiers	188
Distortion in Radio-frequency Amplifiers	193
Current Amplification	194
Limit of Amplification	196
Theory of Inverse Feedback Amplifiers	197
Inverse Feedback Circuits	204
Use of Inverse Feedback to Obtain High Selectivity	208
Use of By-pass Condensers	209
Use of Vacuum Tubes as Variable-impedance Elements	211
Problems	216
Supplementary Bibliography	219

CHAPTER 7

CLASS A AND CLASS AB1 POWER AMPLIFIERS	222
Methods of Analysis of Power Amplifiers	222
Power Relations in Vacuum-tube Plate Circuits	223
Plate-circuit Efficiency	224
Power Output	225
Optimum Power Output	226
Class A Power Amplifiers	226
Triode Class A1 Power Amplifiers	227
Theoretical Value of Triode Optimum Load and Power	228
Optimum Power Output in Terms of Operating Plate Voltage	233
Theoretical Plate-circuit Efficiency	233
Limitation of Power Output by Plate Dissipation	234
Determination of Power-triode Operating Conditions and Performance	235
Class A Tetrode and Pentode Power Amplifiers	238
Turn Ratio of Output Transformer	244
Analysis of Push-pull Power Amplifiers	246
Class A1 and Class AB1 Push-pull Triode Amplifier	252
Push-pull Pentode Power Amplifiers	256

	PAGE
Turn Ratio of Output Transformer. Plate-to-plate Load	257
Problems.	258
Supplementary Bibliography	259

CHAPTER 8

CLASS B AND CLASS AB2 AMPLIFIERS	261
Class B Audio-frequency Amplifiers.	261
Class B Characteristics.	263
Harmonic Content of Class B Amplifiers.	265
Power Output of Class B Amplifiers.	266
Power Input, Plate Dissipation, and Plate-circuit Efficiency	267
Use of Hyperbolas in the Determination of Power and Efficiency	268
Determination of Optimum Load	269
Problems of Class B Amplification.	273
Class AB2 Operation	279
Inverse-feedback Class B and Class AB Amplifiers	280
Class C Amplification	280
Problems.	281
Supplementary Bibliography	281

CHAPTER 9

MODULATION AND DETECTION.	283
Modulation.	283
Amplitude Modulation.	284
Side Frequencies in Amplitude Modulation.	286
Amplitude Modulation by Curvature of Tube Characteristics.	287
Balanced Modulator.	291
Amplitude Modulation by Complete Rectification.	292
Linear Plate and Grid Modulation.	296
Graphical Modulation Analysis.	298
Secrecy Systems (Speech Scramblers)	299
Detection of A-m Waves.	300
Detection by Curvature of Current-voltage Characteristic	301
Analysis of Square-law Detection	302
Frequency Converters.	305
Detection by Complete Rectification.	306
Analysis of Ideal Linear Diode Detection.	309
Detection Efficiency and Effective Input Resistance of the Ideal Linear Diode Detector.	312
Linear Diode Detection of the Sum of Two Voltages of Different Frequencies	314
Effect of Curvature of Diode Characteristic	317
Design of Practical Diode Detectors.	317
Linear Plate Detection (Linear Transrectification).	320
Linear Grid Detection.	320
Graphical Detection Analysis.	322
Series Expansion and Equivalent Circuit for Detection.	323
Radio Communication by Means of A-m Waves	325
Automatic Gain (Volume) Control (A.V.C.)	326
Frequency Modulation.	327
Phase Modulation.	331

CONTENTS

XV

	PAGE
F-m Circuits	331
Detection of F-m Voltage	333
Interference Suppression	336
Interference-to-signal Ratio in A-m Systems	337
Interference-to-signal Ratio in F-m Systems	338
Use of Preemphasis	340
Static Interference	341
Interference Caused by Carrier or Static of High Amplitude	343
Advantages and Disadvantages of Frequency Modulation in Radio Com- munication	343
Problems	345
Supplementary Bibliography	346

CHAPTER 10

TRIGGER CIRCUITS, PULSE GENERATORS, AND OSCILLATORS	349
Trigger Circuits	349
Applications of Trigger Circuits	356
Circuits for Generating Triggering Pulses	357
Rectangular-wave and Rectangular-pulse Generators	359
Vacuum-tube Oscillators	360
Relaxation Oscillators	361
The Multivibrator	362
Van der Pol Relaxation Oscillator	365
Relaxation Oscillators for the Generation of Saw-tooth Waves	366
Use of Relaxation Oscillators in Frequency Transformation	369
Analysis of Multivibrator Frequency Control	371
Analysis of Sine-wave Oscillators	372
Theory of Negative-resistance Oscillators	373
Negative-resistance Oscillator Circuits	380
Feedback Oscillators	387
Generalized Feedback Oscillator Circuit	392
Use of Self-bias to Limit Amplitude of Oscillation	393
Resistance-capacitance-tuned Oscillators	396
Wave Form and Frequency Stability of Feedback Oscillators	401
Effect of Load upon Frequency. Use of Buffer Amplifier and Electron Coupling	403
Resistance Stabilization	405
Impedance Stabilization	406
Crystal Oscillators	408
Magnetostriction Oscillators	409
Power Output of Oscillators	411
Beat-frequency (Heterodyne) Oscillators	412
Problems	414
Supplementary Bibliography	415

CHAPTER 11

ELECTRICAL CONDUCTION IN GASES	416
Current-voltage Characteristics of Glows	416
Physical Aspects of Glow Discharge	418
Potential Distribution in the Glow Discharge	420
"Normal" and "Abnormal" Glow	421

	PAGE
Theory of Glow Ignition	422
Time Required for Ignition	427
Paschen's Law	427
Glow Breakdown	429
Distinction between Ignition and Breakdown Voltage	431
Application of the Current-voltage Diagram	432
Dynamic Current-voltage Characteristics	433
Grid Control of Glow Discharge	436
Theory of Arc Discharges	438
Arcs with Separately Heated Cathodes	440
Grid Control of Arcs	441
Magnetic Control of Arcs	444
Igniter Control of Arcs	445
Deionization	446

CHAPTER 12

GLOW- AND ARC-DISCHARGE TUBES AND CIRCUITS	448
Essential Facts Concerning Glow and Arc Discharges	448
Applications of Glow Tubes	449
The Glow-discharge Tube as a Light Source	449
The Glow-discharge Tube as a Voltage Stabilizer	452
The Glow-discharge Tube as a Rectifier	453
The Glow-tube Relaxation Oscillator	454
The Grid-glow Tube	458
Grid-glow-tube Circuits	459
Starter-anode Glow Tubes	461
Arc-discharge Tubes	462
Advantages of Arc-discharge Tubes	463
Tungar Rectifier	463
Cathode Structure of Low-pressure Hot-cathode Arc Tubes	464
Choice of Gas or Vapor	466
Arc-tube Ratings and Definitions	467
Grid Current Previous to Firing	468
Electrode Structure and Characteristics of Thyratrons	469
Comparison of Thyratrons and High-vacuum Tubes	473
Precautions Required in the Use of Arc Tubes	475
Applications of Hot-cathode Arc-discharge Tubes	475
Hot-cathode Arc Tube as a Light Source	475
Hot-cathode Arc Diode as a Rectifier	476
Arc Tube as a Control Device. D-c Operation	476
Parallel Control	477
Series Control	479
Relaxation Control	480
Counter-e.m.f. Control	484
Parallel Switching Circuits. High-speed Counting Circuits	486
Thyratron Saw-tooth-wave Generator	488
Thyratron Inverters	491
D-c Transformer	501
Thyratron Motors	503
The Use of Arc Tubes as Amplifiers	505
A-c Operation of Thyratrons. Phase Control	505

CONTENTS

xvii

	PAGE
Phase-control Circuits	509
Use of Saturable Reactor in Phase-control Circuits	515
Voltage Impulses for Grid Control	516
Applications of A-c-operated Control Circuits	517
Welding Control	520
Mercury Pool Arc-discharge Tubes	522
Comparison of Igniter and Grid Control	523
Ignitron Structure	525
Ignitron Circuits	526
Externally Controlled Mercury Pool Arc Tube	528
The Strobotron	528
Stroboscopes	529
Problems	532

CHAPTER 13

LIGHT-SENSITIVE TUBES AND CELLS	533
Types of Photoelectric Phenomena	533
Laws of Photoelectric Emission	534
Definitions	535
Current-wave-length Characteristics	536
Types of Phototubes	538
Characteristics of Vacuum Phototubes	538
Phototube Sensitivity	539
The Gas Phototube	540
Phototube Circuits	543
Sensitivity of Phototube and Direct-coupled Amplifier	548
The Anode Diagram	549
Design of Phototube Circuits	550
Secondary-emission Multipliers	551
Photoconductive Cells	553
Photovoltaic Cells (Barrier-layer Cells)	556
Problems	560
Supplementary Bibliography	561

CHAPTER 14

POWER SUPPLIES	564
Definitions	564
Basic Rectifier Circuits	565
Factors Affecting Choice of Rectifier Tubes and Circuits	567
Characteristics of Rectifier Circuits	569
Current Wave Form	572
Smoothing Filters	574
Analysis and Design of Condenser Filters	575
Illustrative Problem	581
Analysis and Design of Choke-condenser (L-section) Filters	582
Illustrative Problem	589
Choke-condenser Filter with Condenser Input	590
Voltage Stabilizers	590
Current Stabilizer	594
Problems	595
Supplementary Bibliography	595

CHAPTER 15

	PAGE
ELECTRON-TUBE INSTRUMENTS AND MEASUREMENTS	597
Vacuum-tube Voltmeters	597
Use of Transfer Characteristics in Voltage Measurement	598
Plate-detection (Transrectification) Voltmeters	598
Balanced Plate Circuits	602
Diode Voltmeters	604
Grid-detection Voltmeter	607
Logarithmic Voltmeter	608
Voltmeters Based on Voltage or Current Amplifiers	609
Slide-back Voltmeters	610
Inverted Voltmeter	612
Vacuum-tube Ammeters	612
Vacuum-tube Wattmeter	618
Vacuum-tube Ohmmeters	619
Time and Speed Meters	620
Counting Circuits	623
Frequency Meters	624
Cathode-ray Oscillographs (Oscilloscopes)	628
Deflection of Electron Beam	630
Cathode-ray Tube Screens	633
Oscilloscope Time Bases	634
Oscilloscope Amplifiers	638
Electronic Switches for the Observation of Two Waves	639
Electronic Transient Visualizers	641
Oscillographic Comparison of Frequencies	644
Effect of Capacitance of Deflecting Plates	647
Electron-ray Tube	648
Determination of Static Tube Characteristics	649
Dynamic Measurement of Tube Factors	650
Tube-factor Bridges	651
Harmonic Analyzers	659
Measurement of Voltage Amplification	665
The Use of Triangular and Rectangular Waves in Amplifier Analysis	666
Measurement of Power Output	667
Determination of Optimum Power Output and Optimum Load	668
Problem	669

APPENDIX

PARALLEL EQUIVALENT CIRCUITS	671
POWER RELATIONS IN VACUUM-TUBE PLATE CIRCUITS	672
LINEAR MODULATION	673
CHART FOR THE DETERMINATION OF REACTANCE	675
CHART FOR THE DETERMINATION OF DECIBEL GAIN	676
CONVERSION-FACTOR CHART FOR POWER TUBES	677
PLATE CHARACTERISTICS OF TYPICAL AMPLIFIER TUBES	678

CONTENTS

xix

	PAGE
OPERATION CHARACTERISTICS OF TYPICAL RECTIFIER TUBES	683
RECTIFICATION CHARACTERISTICS FOR A TYPICAL DIODE DETECTOR TUBE . . .	684
OPERATING DATA FOR TYPICAL RECEIVING TUBES.	685
OPERATING DATA FOR TYPICAL POWER THYRATRONS.	686
OPERATING DATA FOR TYPICAL IGNITRONS	688
AUTHOR INDEX	689
SUBJECT INDEX.	697
SYMBOL INDEX	709
PROBLEM ANSWERS	713